

1 SI Units

Monday, January 7, 2019

3:04 PM

- EE deals with systems that produce, transmit, and measure electronic signals.

◦ Five major categories

Computer system, Control system, Power system, Signal processing system


...

- SI Units (The International System of Units)

Quantity	Basic Unit	Symbol
Mass	kilogram	kg
Time	second	s
Length	meter	m
Temperature	Kelvin	K
Luminous intensity	Candela	cd
Electric current	ampere	A
Amount of substance	mole	mol

- There're also derived units in SI


- Electric charge, unit: Coulomb C
- Current $I = \text{charge}/s$
Charge of an electron: $1.6 \cdot 10^{-19}$
- Ideal circuit component
 - Def: a mathematical model of an actual electrical component
- Physical prototype
 - An actual electric system
- Electric Charge
 - Electric Charge is discrete, quantized
 - Smallest unit of electric charge = $1.6 \cdot 10^{-19} \text{ C}$
 - Consequence of charges in motion: Electric fluid(current) \rightarrow Magnetic field
 - Bipolar "+" or "-"
 - To separate charges - Electric force(voltage)
- Electric Current
 - Def: the time rate of transfer of electric charges across a specific boundary
 - $I(t) = dq/dt$
 - Unit: Ampere(A) or Coulomb(C)/Second(s)
 - Direct current(DC): current flow in one direction
 - Alternating current(AC)

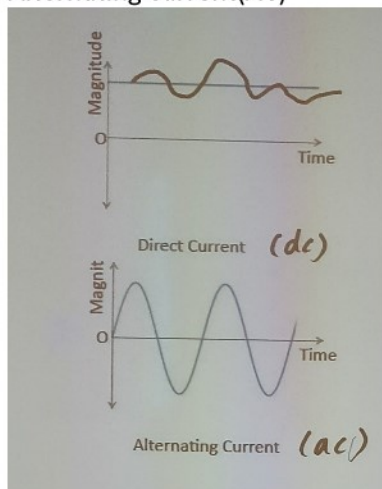

- $q = 10 - 10e^{-2t} \text{ mC}$, find i at $t = 1.0 \text{ s}$.
 $t = 0, q = 0$ $i = \frac{dq}{dt} = 20e^{-2t} = 20e^{-2} \text{ mC/s} = 20e^{-2} \text{ mA}$



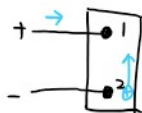- Voltage: the energy per unit charge created by the separation
 - $V_{12} = V_1 - V_2$



- Voltage: Energy needed to move one unit of positive charge from the negative

terminal to the positive terminal

- $V = dW/dq$
W: joules(J)
q: Coulombs(C)
- E.g. An energy source forces a constant current of 2A for 10 s to flow through a light bulb, resulting in 2.3 kJ that is given off in the form of light and heat energy. Calculate the voltage drop across the light bulb.

$$q = it = 2A \cdot 10s = 20As$$

$$V = \frac{2.3 \times 10^3 J}{20 As} = 115V$$

- Ideal Basic circuit element
 - Def:
 - Has only two terminals, which are points of connection to other circuit components
 - Cannot be subdivided into other elements
 - Can be described mathematically in terms of current &/| voltage
 - Five ideal basic circuit elements
 - Ideal voltage source
 - Ideal current source
 - Resistor
 - Capacitor
 - Inductor
- Passive Sign Convention
 - Whenever the reference direction for the current in an element is in the direction of the reference voltage drop across the element, use a '+' in any expression that relates the voltage to the current. Use '-' otherwise.

3. power

Thursday, January 10, 2019

7:49 PM

- $p = \frac{dw}{dt} = v\dot{w} = \left(\frac{dw}{dq} \cdot \frac{dq}{dt}\right)$

- When using passive sign convention, $p = v\dot{w}$

When current reference is in the direction of a reference voltage rise, $p = -v\dot{w}$



- Interpreting p .

(dissipating power)


- $p > 0$, power is delivered to the circuit element.

- $p < 0$, power is being extracted from the circuit element.

(generating power)

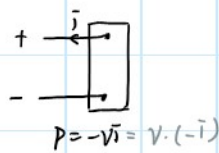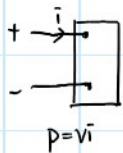

- e.g.

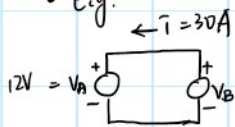

Power goes from A to B.

$$P_A = 30A \times 12V$$

HW1

Wednesday, January 16, 2019 12:58 PM

Review | Constants

The numerical values for the currents and voltages in the circuit in (Figure 1) are given in the table below.

Element	Voltage (V)	Current (mA)
a	-18	-86
b	-18	45
c	2	-41
d	20	-55
e	16	-14
f	36	31


Review | Constants

The numerical values for the currents and voltages in the circuit in (Figure 1) are given in the table below.

Element	Voltage (V)	Current (mA)
a	-18	-86

Figure

< 1 of 1 >

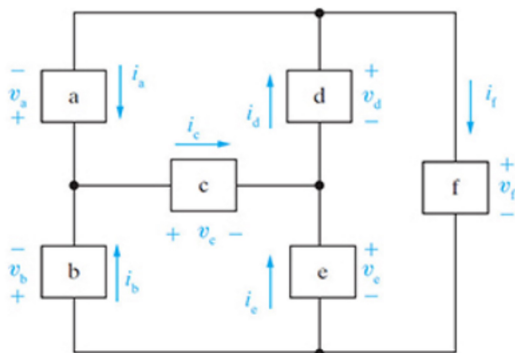

Part A

Find the total power developed in the circuit.

Express your answer to three significant figures and include the appropriate units.

View Available Hint(s)

$p = 2440 \text{ mW}$

Submit

Previous Answers

✓ Correct

Here we learn how to determine the total power developed in the circuit using the power equation convention.

magnitude of
the power generated
or the power dissipated.

Rem: add up the values with the same
sign.


Review | Constants

The voltage and current at the terminals of the circuit element in (Figure 1) are zero for $t < 0$.

$$v = (1500t + 1)e^{-750t} \text{ V}, \quad t \geq 0;$$

$$i = 50e^{-750t} \text{ mA}, \quad t \geq 0.$$

Figure

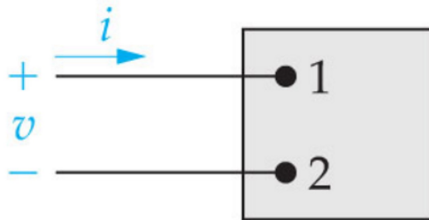

$$P_{\max} = 50.0 \text{ mW}$$

Submit

[Previous Answers](#)

✓ Correct

$$P = vi = 75te^{-1500t} + 0.05e^{-1500t}$$

$$\therefore P \downarrow$$

$$\therefore t=0, P_{\max} = 0.05 \text{ W}$$

Part C

Find the total energy delivered to the circuit element in microjoules.

Express your answer using three significant figures.

$$w = 66.7 \text{ } \mu\text{J}$$

Submit

[Previous Answers](#)

✓ Correct

$$W_{\text{tot}} = \int_0^{\infty} (75te^{-1500t} + 0.05e^{-1500t}) dt$$

$$= \left[\frac{75te^{-1500t}}{-1500} - \frac{75e^{-1500t}}{1500^2} + \frac{0.05e^{-1500t}}{-1500} \right]_0^{\infty}$$

$$= \frac{75}{1500^2} + \frac{0.05}{1500} = 66.7 \text{ } \mu\text{J}$$

$$\lim_{t \rightarrow \infty} \frac{t e^{-1500t}}{e^{-1500t}} = \frac{1}{1500e^{1500t}} = 0$$