

5.1-4

Friday, February 22, 2019


2:31 PM

- Op-amp (operational amplifier)

- op-amp is a voltage amplifier with high gain


- op-amp { Saturation
Linear

*A/D converters
Comparator*

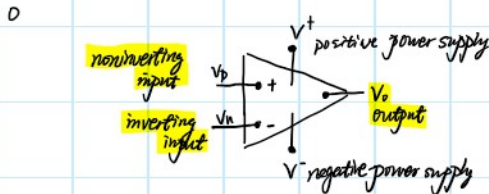

■ The output voltage of an op-amp can't be arbitrarily high

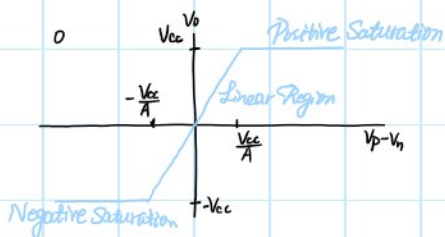Limit: Power supply. (Energy Conservation)



$$V_o = \begin{cases} -V_{cc} & A(V_p - V_n) < -V_{cc} \\ A(V_p - V_n) & -V_{cc} \leq A(V_p - V_n) \leq V_{cc} \\ V_{cc} & A(V_p - V_n) > V_{cc} \end{cases}$$

o In a ideal op amp, the gain \$A\$ is infinite, in a practical op amp

$$A \geq 10000$$

∴ o $V_p = V_n$ Voltage constrain

e.g. Consider an op amp with \$V^+ = 12V\$, \$V^- = -12V\$, \$A = 2 \times 10^6\$

(a) If \$V_p = 0.1\$, \$V_n = 0V\$, calculate \$V_o\$.


(b) What's the max \$V_p\$ in linear region?

(a) $A \cdot (V_p - V_n) = 2 \times 10^6 > 12V$

∴ 12V

(b) $A \cdot V_p < 12V$

$V_p < 60mV$

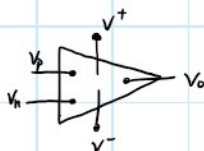

$$V_p < 60 \text{ mV}$$

o Use negative feedback to achieve linear operation.

- first assume linear, then check if it stands.

If $V_p - V_n$ is too positive, $V_o \uparrow$, $V_n \uparrow$, $(V_p - V_n) \downarrow$


If $V_p - V_n$ too negative, $V_o \downarrow$, $V_n \downarrow$, $(V_p - V_n) \uparrow$




o $i_p = i_n = 0$ (input $R \rightarrow \infty$ if ideal)

$$i_o = -(i_c + i_c^-)$$

$$i_p + i_n + i_c + i_c^- + i_o = 0$$

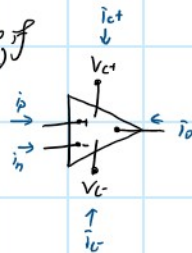

• The inverting - Amplifier circuit

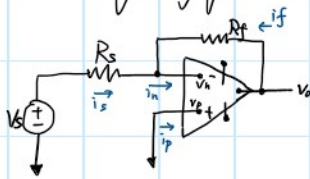

$$\therefore V_p = 0 \quad \therefore V_n = 0$$

$$i_n = i_f + i_s = 0, \quad i_s = \frac{V_s}{R_s}, \quad i_f = \frac{V_o}{R_f} \rightarrow A = \frac{V_o}{V_p - V_n}$$

$$\Rightarrow V_o = -\frac{R_f}{R_s} \cdot V_s = A(V_p - V_n)$$

$$A = \frac{V_o}{V_s} = -\frac{R_f}{R_s}$$

➔ The sign of the output voltage is inverted, and the magnitude


is scale by $\frac{R_f}{R_s}$

e.g. find the range of V_s without saturating the inverting amp

$$-20 \leq \frac{R_f}{R_s} \cdot V_s \leq 10$$

$$-20 \leq -5V_s \leq 10$$

$$-2 \leq V_s \leq 4$$

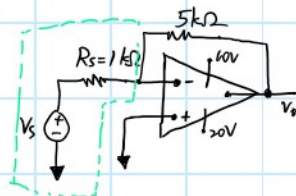

Sometimes need to do source

transformation to do this.

• The summing amplifier circuit


$$i_1 + i_2 + i_3 + \dots + i_n = 0$$

• The summing amplifier circuit

$$i_a + i_b + i_c + i_f = i_n = 0$$

$$V_n = V_p = 0$$
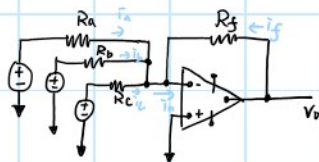
$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} + \frac{V_o}{R_f} = 0$$



$$\Rightarrow V_o = -R_f \left(\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right) \Rightarrow \text{Inverting summing amplifier equation}$$

$$\text{if } R_a = R_b = R_c = R_s \Rightarrow$$

$$V_o = -\frac{R_f}{R_s} (V_a + V_b + V_c)$$

e.g. design an opamp that V_a, V_b, V_c, V_d are the 1, 2, 3, 4th digit

below decimal pts of V_o . e.g. $V_a=1, V_b=2, V_c=3, V_d=4, V_o=0.1234$


$$V_o = -R_f \left(\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} + \frac{V_d}{R_d} \right)$$

$$R_f : R_a : R_b : R_c : R_d$$

$$= 1 : 10 : 100 : 1000 : 10000$$

To invert the sign, cascade with an inverting amplifier with $R_s = R_f$.

• Non-inverting Amplifier Circuit

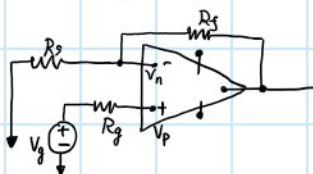

$$i_p = i_n = 0 \text{ (consider as open circuit)}$$

$$V_n = V_p = V_g$$

$$V_o = \frac{R_s + R_f}{R_s} V_g$$

$$V_n = V_g \cdot \frac{R_s}{R_s + R_f}$$

e.g. assume the op-amp ideal


(a) find output voltage when $R_x = 60k\Omega$

(b) Find max of R_x if not saturate.

$$(a) V_p = \frac{R_x}{R_x + 5k} \cdot 0.4V = 0.32V$$

$$V_o = \frac{63k + 4.5k}{4.5k} \cdot 0.32V$$

$$= 4.8V$$

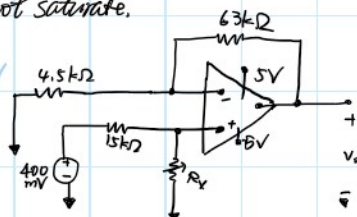

$$(b) V_p = \frac{R_x}{R_x + 5k} \cdot 0.4V$$


$$V_o = \frac{63k + 4.5k}{4.5k} \cdot 0.4V \cdot \frac{R_x}{R_x + 15k} \approx 5$$

$$R_x \leq 0.83(R_x + 15k)$$

$$R_x \leq 75k\Omega$$

(max)

The Difference-Amplifier Circuit

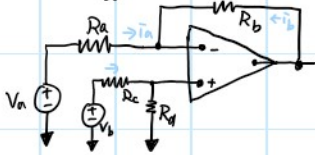

$$i_n = i_a + i_b = 0$$

$$\frac{V_a - V_n}{R_a} + \frac{V_o - V_n}{R_b} = 0 \quad \dots (1)$$

$$V_p = \frac{R_d}{R_c + R_d} V_b = V_n \quad \dots (2)$$

$$(1) \quad \frac{V_o}{R_b} = V_n \left(\frac{1}{R_a} + \frac{1}{R_b} \right) - \frac{V_a}{R_a}$$

Difference amplifier equation (1,2)


$$V_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} V_b - \frac{R_b}{R_a} V_a$$

o If we want $\frac{R_d}{R_a} \cdot \frac{(R_a + R_b)}{(R_c + R_d)} = \frac{R_b}{R_a}$

$$V_o = \frac{R_b}{R_a} \cdot \left(1 + \frac{R_b}{R_a} \right) \frac{1}{1 + \frac{R_b}{R_a}} V_b - \frac{R_b}{R_a} V_a$$

$$\Rightarrow \text{Set } \frac{R_a}{R_b} = \frac{R_c}{R_d}, \text{ then } V_o = \frac{R_b}{R_a} (V_b - V_a)$$

e.g. Power absorbed by the 4 k Ω ?

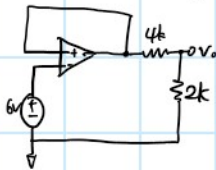

$$V_p = V_n = 6V$$

\therefore 6V, 4k, 2k form a circuit.

$$\frac{6 - V_o}{4k} = \frac{V_o}{2k}$$

$$\therefore V_o = 2V$$

$$P = V^2 / R = \frac{4^2}{4k} = 4mW$$


Prob

Monday, February 25, 2019

4:59 PM

■ Review | Constants

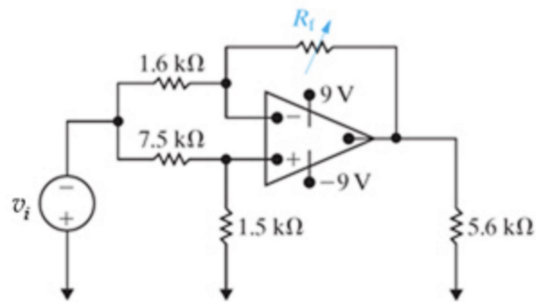The resistor R_f in the circuit in the figure is adjusted until the ideal op amp saturates. (Figure 1)



Specify R_f , given that $v_i = 15 \text{ V}$.

Express your answer with the appropriate units.

$R_f = 1.47 \text{ k}\Omega$

Submit

[Previous Answers](#)

✓ Correct

$$V_o = 9 \text{ V} \quad V_p = V_n$$

$$\frac{V_p}{1.5 \text{ k}} + \frac{V_p - (-15 \text{ V})}{7.5 \text{ k}} = 0$$

$$5V_p + V_p + 15 = 0 \\ V_p = -2.5 \text{ V}$$


$$\therefore V_n = -2.5 \text{ V}$$

$$\therefore \frac{V_n - (-15 \text{ V})}{1.6 \text{ k}} + \frac{V_n - V_o}{R_f} = 0$$

$$\frac{-2.5 + 15}{1.6} = \frac{9 + 2.5}{R_f}$$

$$R_f = 1.472 \text{ k}\Omega$$

Find the Norton equivalent with respect to the terminals a,b for the circuit in if $v = 20\text{ V}$, $i = 5\text{ A}$.

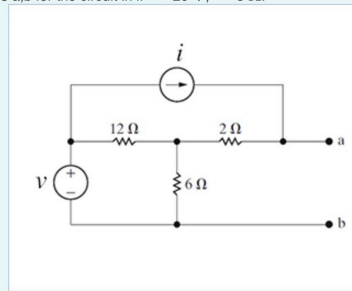

Approach I.

Mesh Current $\Rightarrow i_{sc}$

Deactivate all independent sources $\Rightarrow R_{th}$

$$i_{sc} \cdot R_{th} = V_{oc}$$

Approach II.

$Y \rightarrow \Pi$

